
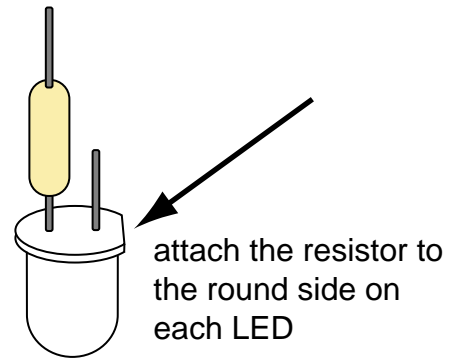


PASSIVE A/B SWITCHER

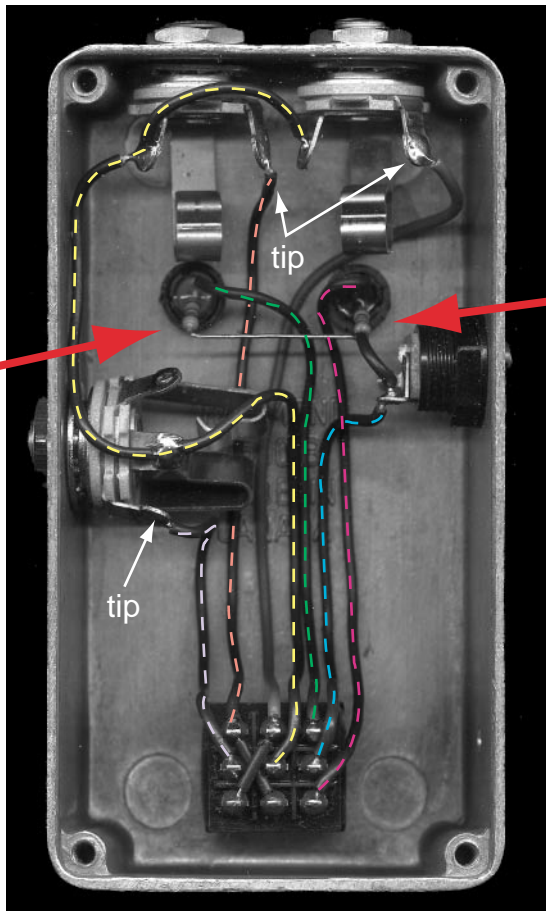There is an inherent problem with most A/B Boxes when running separate effects for each channel. Most A/B Boxes do not ground out the channel not being used, resulting in massive hum + hiss when distortion or fuzz pedals are left on. This design eliminates that problem, and has the purest, non buffered, most transparent tone available.



- www.MOUSER.com (800)346-6873
- | | |
|----------------------------|------------|
| HAMMOND1590B BOX | 546-1590B |
| Yellow LED | 604-L53YD |
| Red LED | 604-L53HD |
| LED Holder | 606-4304MC |
| 2.1mm DC Jack | 163-4302 |
| Switchcraft Mono Jack | 502-11 |
| Switchcraft Stereo Jack | 502-12B |
| (only for battery powered) | |
- FULLTONE 3PDT SWITCH (available at fulltone.com)



10K 1/4 watt resistor

2.2K 1/4 watt resistor

