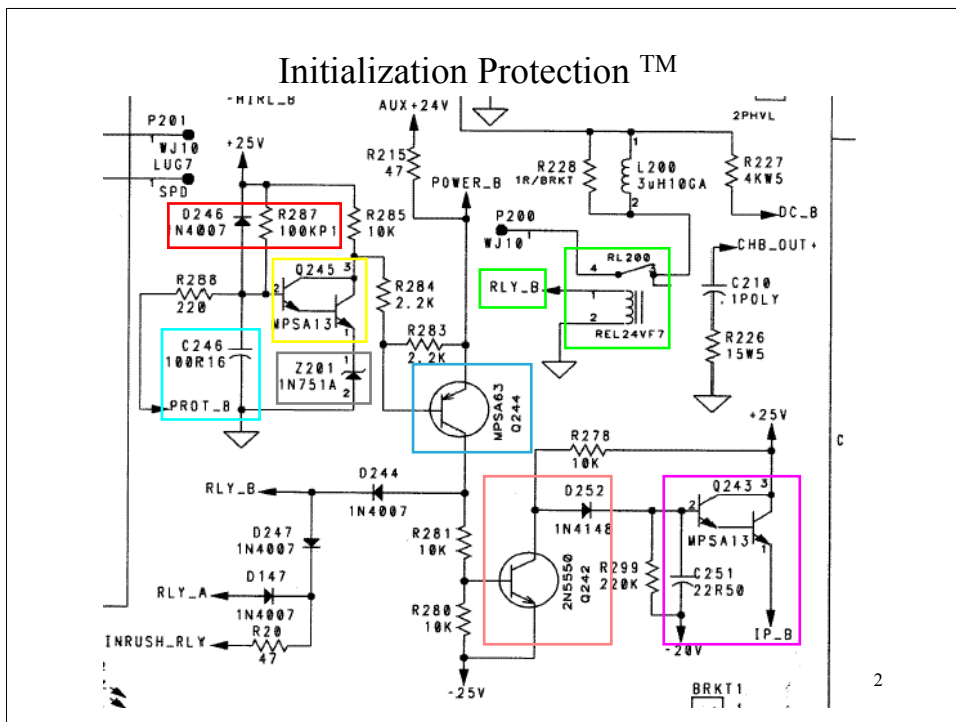


GPS2600 - 3500

Larry Cook
Peavey Electronics Instructor




When power is applied to the GPS3500, **RL200** isolates the amplifier from the speakers. Initially, **Q245** has zero volts between the base emitter and will be off. Since **Q245** is off **Q244** will be off and **RLY_B** will be low. While **RLY_B** is low the **RL200** will be off.

C246 will initially have zero volts across it. It will start charging through **R287**. **Z201** is a 5 volt zener so **Q245** will not turn on until **C246** charges to about 6.5 volts. Once **Q245** turns on the voltage at the base of **Q244** is reduced to about 5 volts. This turns **Q244** on and applies about 24 volts to **RL200**. Note during power off **C246** discharges through **D246** so the relay opens quick.

Initially **Q242** is off and the voltage across **C251** is zero. There will be -20 volts at the base of **Q243** and it will be off. While **Q242** is off, **C251** will charge up and **IP_B** will increase to +25 volts. Once the relay is energized, **Q242** will turn on. **D252** will force **C251** to discharge only through the base emitter of **Q243** and **IP_B** will slowly decrease to zero volts. When **IP_B** is high the input is muted. When it is low the input is not muted.

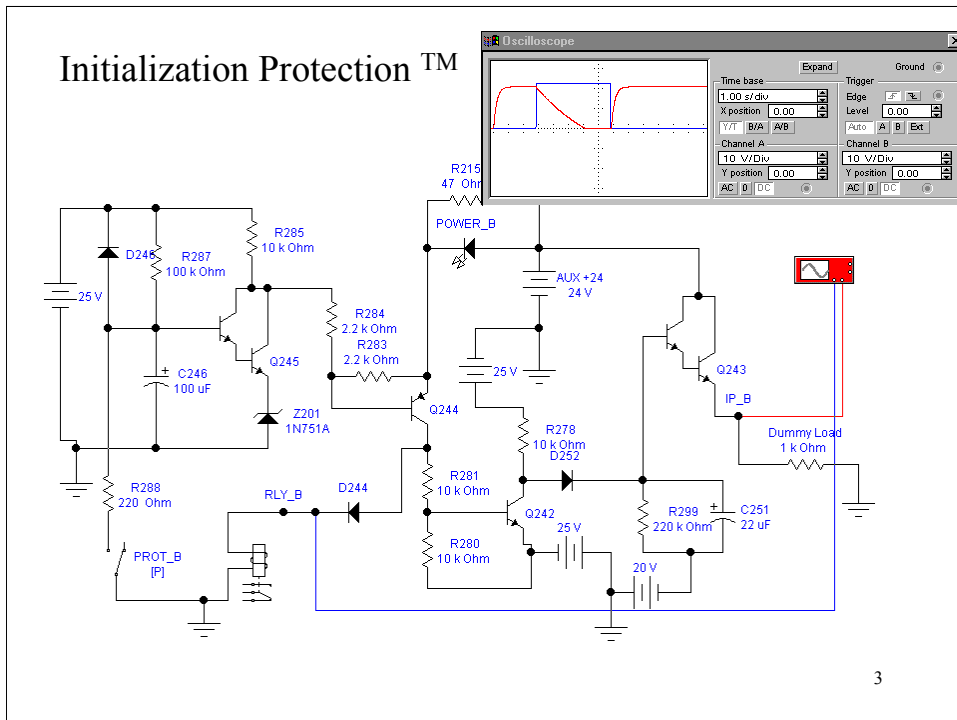Notice if **PROT_B** goes low the relay will open and the cycle starts over.




When power is applied to the GPS3500, RL200 isolates the amplifier from the speakers. Initially, Q245 has zero volts between the base emitter and will be off. Since Q245 is off Q244 will be off and RLY_B will be low. While RLY_B is low the RL200 will be off.

C246 will initially have zero volts across it. It will start charging through R287. Z201 is a 5 volt zener so Q245 will not turn on until C246 charges to about 6.5 volts. Once Q245 turns on the voltage at the base of Q244 is reduced to about 5 volts. This turns Q244 on and applies about 24 volts to RL200. Note during power off C246 discharges through D246 so the relay opens quick.

Initially Q242 is off and the voltage across C251 is zero. There will be -20 volts at the base of Q243 and it will be off. While Q242 is off, C251 will charge up and IP_B will increase to +25 volts. Once the relay is energized, Q242 will turn on. D252 will force C251 to discharge only through the base emitter of Q243 and IP_B will slowly decrease to zero volts. When IP_B is high the input is muted. When it is low the input is not muted.

Thermal Protection DC Protection

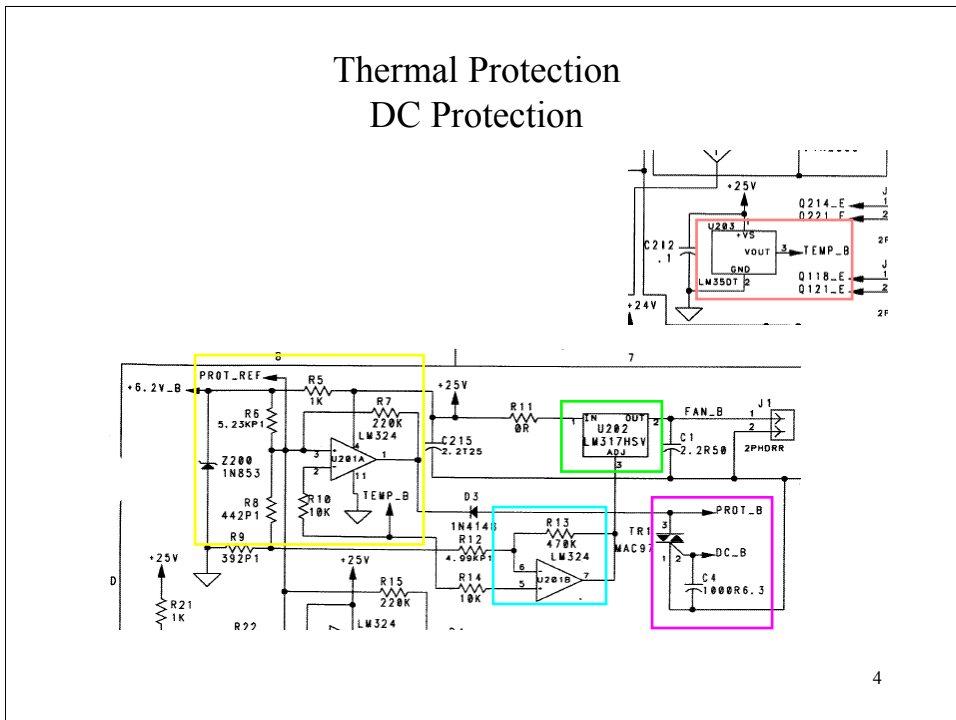


U203 is a precision centigrade temperature sensor. It's output will be 10mv for each degree centigrade. **U202** is a three terminal voltage regulator. It's output is 1.25 volts higher than the voltage on the **ADJ** pin. **U202** directly controls the speed of the fan. The **TEMP_B** signal is applied to **U201B** which controls the fan speed through **U202**. **R13** provides hysteresis. The fan will stop at a lower temperature than it started.

If **TEMP_B** becomes greater than **PROT_REF**, then the output of **U201** will go low and **PROT_B** will go low. This will cause the initialization protection to open the relay and system initialization will start over after the heat sink cools.

DC_B is feedback from the output before the relay. Subsonic frequencies and DC on the output of sufficient strength will cause **TR1** to turn on and **PROT_B** will go low. This will cause the initialization protection to open the relay and system initialization will start over after the fault condition is removed.

Short Circuit Load Fault Protection™

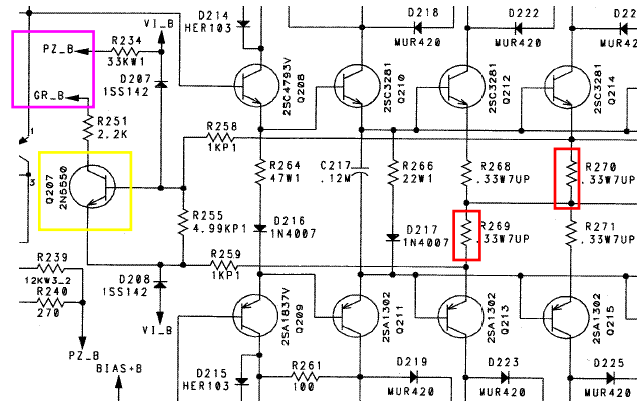


5

GR_B is normally about +25 volts. Excessive current through **R269** or **R270** will indicate a load fault or short. **PZ_B** is feedback from the output. If there is an output voltage (load fault condition) the voltage from **PZ_B** will prevent **Q207** from turning fully on. In this case **GR_B** would reduce the input. Under a short, **Q207** would turn on and the amp will enter the protect mode. This happens through SH_B and PROT_B not shown here.

Notice that **GR_B** will often be a series of pulses since **Q207** will be controlled by the peak currents through **R269** and **R270**.

DDT and Others

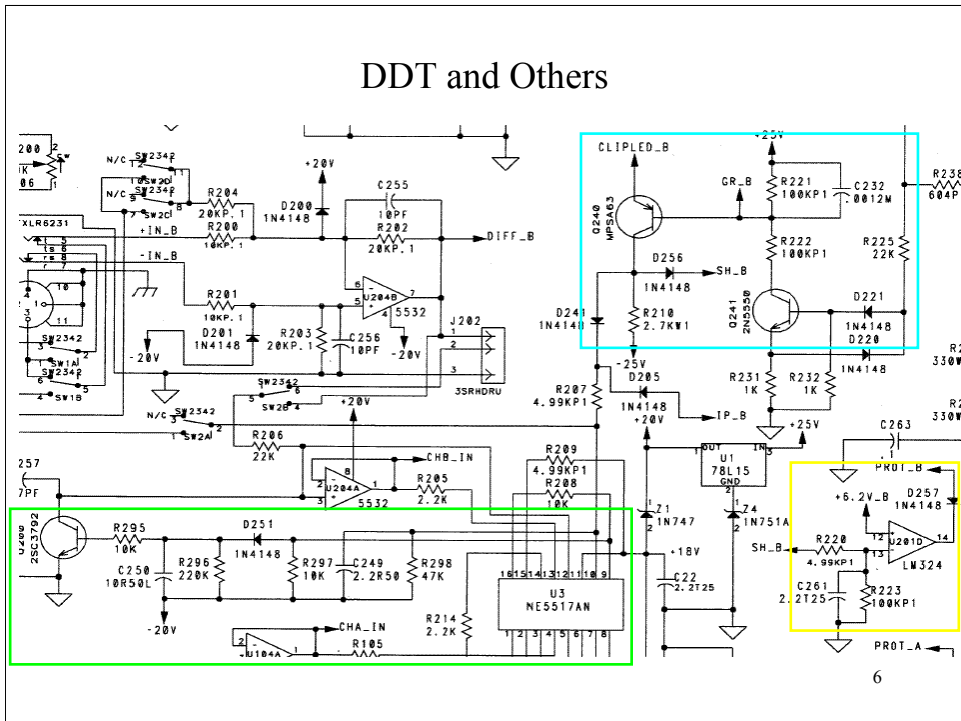

If the frequency and peak voltage of **SH_B** cause **C261** to charge up to greater than 6.2 volts then **PROT_B** will go low the amp will go into protect mode. Initialization will start over if that condition is removed. **SH_B** originates from **Q240** which is controlled by **GR_B** (short and load fault) and **Q241** which detects clipping.

Pin 10 of **U3** is the input to a buffer and **pin 9** is the output. **C249** smoothes the signal providing a DC level instead of pulses. The output on **pin 9** controls the gain of the **OTA** reducing the input appropriately. If the average voltage on **pin 9** becomes large enough then **Q200** will turn on and mute the input.